

ECE 2260 - Fundamentals of Electrical Circuits: Lab 5

Hunter Van Horn

February 19, 2025

Purpose

The purpose of this lab is to simulate and measure the time constant of an RC Circuit


Preliminary

1. In Python, write an analytical solution for $v_o(t)$ (the voltage across the capacitor) assuming V_i is a 0 to 5V step function. Then use Python to graph the function from $t \in [0s, 5\tau]$
2. Using LTspice, create and simulate the RC circuit and use the cursors to identify τ
3. Using the breadboard, build the circuit RC circuit applying 0-5V across using a 100Hz square wave. Measure the time constant using the oscilloscope.

Equipment

- Breadboard
- Multimeter
- Power Supply
- Signal Generator
- Oscilloscope
- Resistor: $10k\Omega$
- Capacitor: $0.1\mu F$

The Circuit

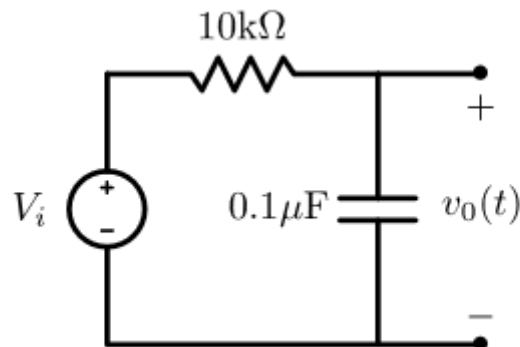

Python Code

Author: Hunter Van Horn, Dexter Ward

Date: 02/06/2025

Dependencies

```
[1]: import numpy as np
import matplotlib.pyplot as plt
```

Voltage Across the Capacitor

```
[2]: def capacitorResponse(vf, vo, t, tau):
    return vf+(vo-vf)*np.exp(-t/tau)
```

This function is used to determine the voltage across the capacitor at any given time (t) provided the time constant (τ) and the initial (V_o) and final (V_f) voltage.

Calculating Tau

```
[3]: def calculateTau(r, c):
    return r*c
```

This function is used to determine the τ of an RC circuit given the resistor and capacitor values.

Finding Tau

```
[4]: def positionAtTau(yVal, vf, vo):
    return np.argmax(yVal > capacitorResponse(vf,vo,1,1))
```

This function can be used to find τ in a given array of voltage values across a capacitor provided V_o and V_f .

This function is able to determine the voltage at $t = \tau$ using the capacitor response function. From there the function utilizes the numpy argmax function to determine the first array position that exceeds the determined voltage.

Graphing

```
[ ]: def graphResponse():
    r = 10000
    c = .0000001
    tau = calculateTau(r,c)
    vf = 5
    vo = 0
    stepSize = .000001
    xVal = np.array([0])
    yVal = np.array([capacitorResponse(vf, vo, xVal[-1], tau)])
```

```


while(xVal[-1] < 5*tau):
    xVal = np.append(xVal, [xVal[-1]+stepSize])
    yVal = np.append(yVal, [capacitorResponse(vf, vo, xVal[-1], tau)])

xVal = xVal*1000

plt.plot(xVal,yVal)
plt.scatter(xVal[positionAtTau(yVal, vf, vo)],yVal[positionAtTau(yVal, vf,
↪vo)])
plt.xlabel('Time (ms)')
plt.ylabel('Voltage (V)')
plt.title('Voltage Across the Capacitor')
plt.grid()
plt.show()


if __name__ == '__main__':
    graphResponse()

```

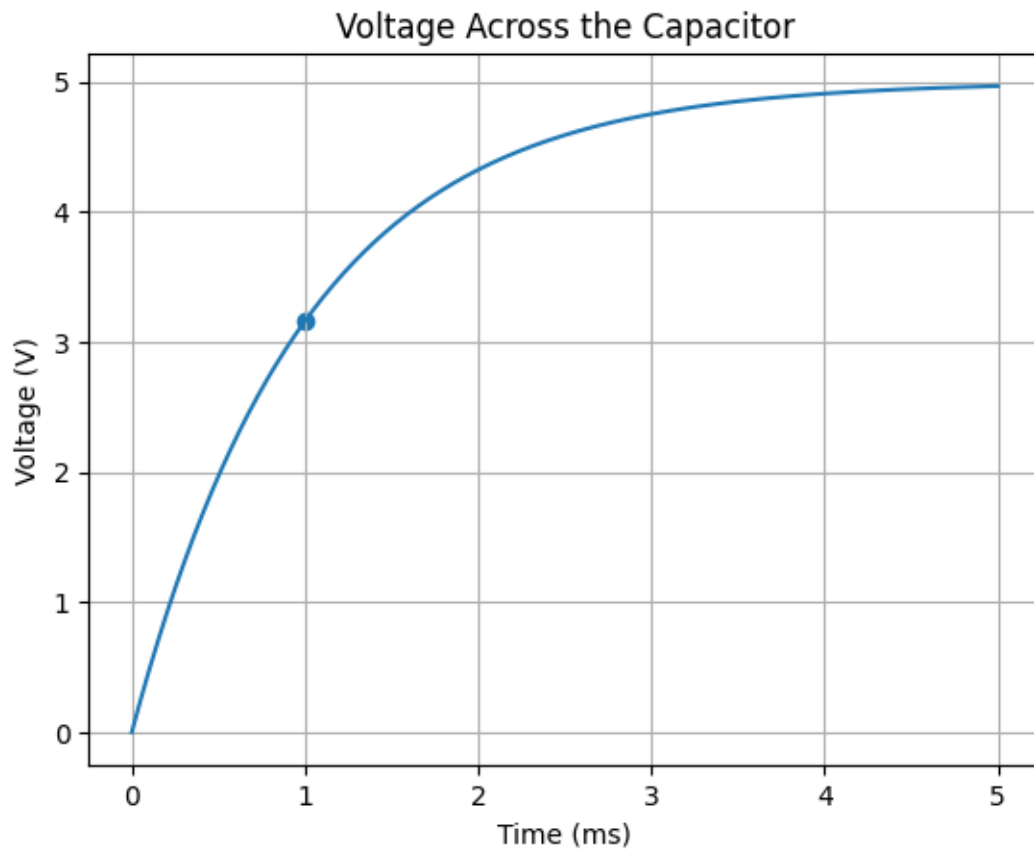

LTspice Simulation

Circuit Diagram

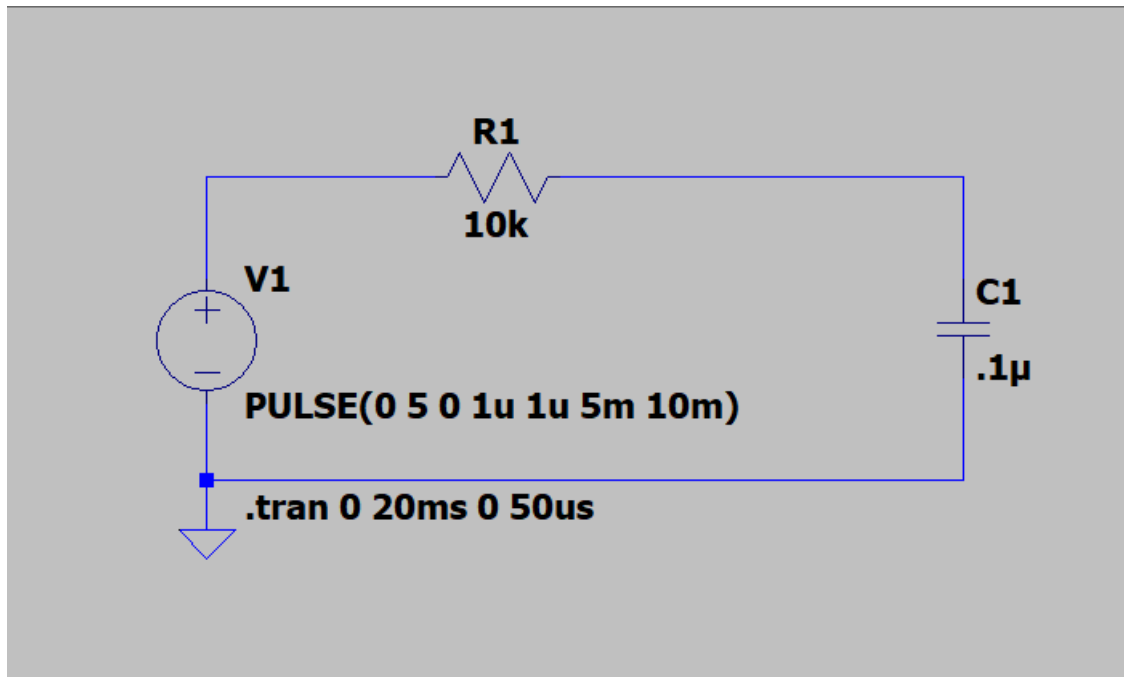

Settings

Independent Voltage Source - V1

Functions

☐ (none)

☒ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)

☐ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)

☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)

☐ SFFM(Voff Vamp Fcar MDI Fsig)

☐ PWL(t1 v1 t2 v2...)

☐ PWL FILE:

Vinitial[V]:

Von[V]:

Tdelay[s]:

Trise[s]:

Tfall[s]:

Ton[s]:

Tperiod[s]:

Ncycles:

Make this information visible on schematic: ☒

DC Value

DC value:

Make this information visible on schematic: ☒

Small signal AC analysis(.AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic: ☒


Parasitic Properties

Series Resistance[Ω]:

Parallel Capacitance[F]:


Make this information visible on schematic: ☒

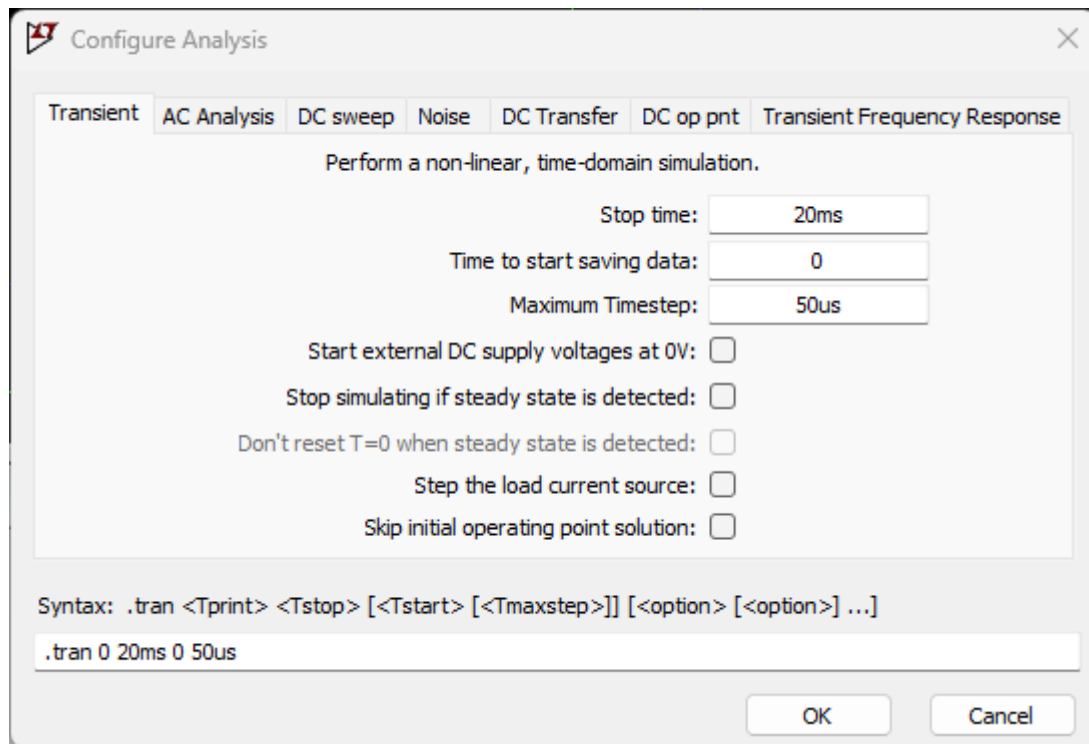This sets the voltage source to a square wave from 0 to 5V with a period of 10ms, an on time of 5ms, and a rise/fall time of 1μs



This sets the oscilloscope output to show two periods with a maximum step size of $50\mu s$

Oscilloscope Trace

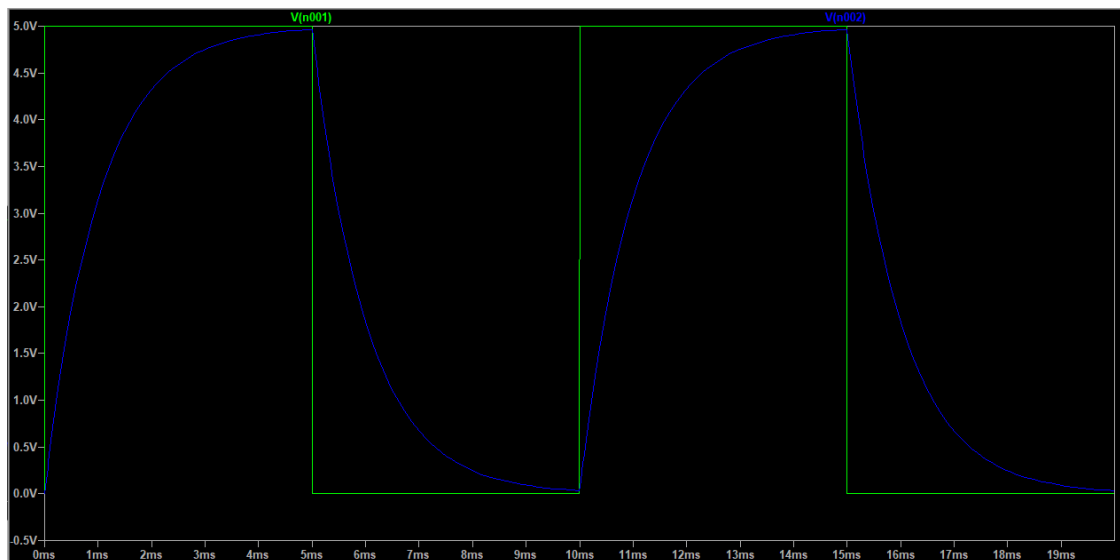

Building the Circuit

